

Question	Answer	Marks
1 (a) (i)	The minimum resistance is when the resistors are all connected in <b>parallel</b> . $R = (10^{-1} + 20^{-1} + 40^{-1})^{-1}$ $R = 5.7 \Omega$	1 1 1
1 (a) (ii)	The maximum resistance is when the resistors are all connected in <b>series</b> . $R = 10 + 20 + 40 = 70 \Omega$	1 1
1 (b)	The resistance of the filament lamp depends on its temperature. At maximum brightness, the resistance of the lamp is a maximum. When the voltage is halved, the resistance of the lamp is not halved because it is a non-ohmic component; hence the current is not halved.	1 1
2 (a) (i) (1)	360 $\Omega$	1
2 (a) (i) (2)	current	1
2 (a) (ii) (1)	$\frac{1}{10} + \frac{1}{20} + \frac{1}{40} = \frac{1}{R}$ $R = 5.7 \Omega$	1 1
2 (a) (ii) (2)	potential difference	1
3 (a)	$R = (100^{-1} + 180^{-1})^{-1}$ $R = 64.3 \Omega$	1 1
3 (b) (i)	p.d. across the resistors = 0.100 $\times$ 64.3 p.d across the resistors = 6.43 V p.d across the LED = 8.2 – 6.43 $\approx$ 1.8 V	1 1 1
3 (b) (ii)	$P = I^2 R = 0.100^2 \times 64.3$ $P = 0.64 \text{ W}$	1 1
4 (a) (i)	<u>Total</u> current into a junction equals the <u>total</u> current out conservation of charge	1 1
4 (a) (ii)	sum of e.m.fs = sum (or total) of p.ds <b>or</b> sum of voltages in (or around) a closed loop in a circuit. energy is conserved	1 1
4 (b) (i)	current in 750 $\Omega = 0.020 \text{ A}$	1
4 (b) (ii)	V across 750 $\Omega = 0.02 \times 750 = 15 \text{ V}$	1
4 (b) (iii)	$R_1 = \frac{45 - 15}{0.03} = 1000 \Omega$ $R_2 = \frac{15}{0.01} = 1500 \Omega$	1 1
5 (a)	R of thermistor decreases as temperature increases supply V is constant because the total R is smaller current increases as $V = IR$	1 1 1
5 (b)	$R_{th} = 40 \Omega$ at 240 $^{\circ}\text{C}$ should be stated or used in calculation total R in circuit = 240 $\Omega$ $I = \frac{6}{240} = 0.025 \text{ A}$ $V = 200 \times 0.025 = 5.0 \text{ V}$	1 1 1 1
5 (c) (i)	correct symbol for LDR	1
5 (c) (ii)	R of LDR decreases as the current in the circuit increases so V increases across the fixed 200 $\Omega$ resistor	1 1
6 (a) (i)	$\frac{12}{2.0} = 6.0 \Omega$	1
6 (a) (ii)	attempt to use resistors in parallel formula $\frac{1}{R} = \frac{8}{6}$ $R = 0.75 \Omega$	1 1 1
6 (a) (iii)	$P = \frac{V^2}{R} = \frac{12^2}{0.75}$ or $8 \text{ V} I = 8 \times 12 \times 2$ or $I^2 R = 16^2 \times 0.75$ $P = 192 \text{ W}$	1 1

Question	Answer	Marks											
6 (b)	$\rho = \frac{RA}{L}$	1											
	$\rho = \frac{6.0 \times 0.24 \times 2.0 \times 10^{-6}}{0.9}$	1											
	$\rho = 3.2 \times 10^{-6}$	1											
	$\Omega \text{ m}$	1											
7 (a)	e.m.f = sum of p.d.s	1											
	$1.5 = 0.50r + (0.50 \times 1.0)$	1											
	$r = 2.0 \Omega$	1											
7 (b) (i)	All values of $I$ are correct	1											
	All values of $P$ are correct												
	<table border="1"> <thead> <tr> <th><math>R / \Omega</math></th> <th><math>I / \text{A}</math></th> <th><math>P / \text{W}</math></th> </tr> </thead> <tbody> <tr> <td>1.0</td> <td>0.50</td> <td>0.25</td> </tr> <tr> <td>2.0</td> <td><math>0.375 \approx 0.38</math></td> <td>0.28</td> </tr> <tr> <td>4.0</td> <td>0.25</td> <td>0.25</td> </tr> </tbody> </table>	$R / \Omega$	$I / \text{A}$	$P / \text{W}$	1.0	0.50	0.25	2.0	$0.375 \approx 0.38$	0.28	4.0	0.25	0.25
	$R / \Omega$	$I / \text{A}$	$P / \text{W}$										
	1.0	0.50	0.25										
2.0	$0.375 \approx 0.38$	0.28											
4.0	0.25	0.25											
		1											
7 (b) (ii)	The power dissipated in maximum when resistance $R$ of the variable resistor is equal to the internal resistance $r$ of the cell.	1											
8 (a)	The resistance between the contacts is very large / infinite.	1											
	Hence the current in the circuit is zero with no p.d. across the $200 \text{ k}\Omega$ resistor.	1											
8 (b)	current = $\frac{6.5}{200 \times 10^3} = 3.25 \times 10^{-5} \text{ A}$	1											
	$R = \frac{9.0 - 6.5}{3.25 \times 10^{-5}}$	1											
	$R = 7.7 \times 10^3 \Omega$	1											
8 (c)	The current in the circuit would be larger.	1											
	The p.d. across the contacts (when in water) would be larger.	1											
	Hence, the voltmeter reading would be smaller.	1											